

Lab3

Single cycle CPU (Simple version)

TA-黃威淳

s094398.cs10@nycu.edu.tw

Notice


- Please fill out the grouping form (Lab 4 ~6)
 - <https://forms.gle/wjPybw6HkHjQTjAd7>
- [Lab 3 討論區](#)
- Lab 3 is **individual work**

Lab 4~6 grouping form




Overview

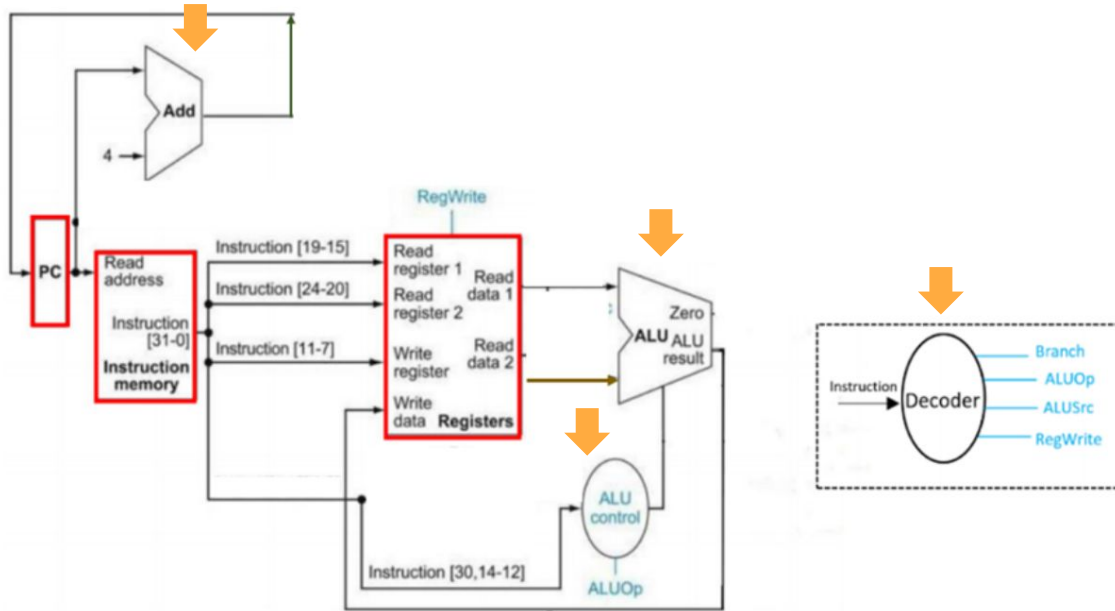- Implement the datapath of Single Cycle CPU as below



Provided

Your work

 

Attached file


- **TODO**
 - **Lab3Code**
 - alu.v
 - Adder.v
 - ALU_Ctrl.v
 - Decoder.v
 - Simple_Single_CPU.v
- **Validate the correction of your implementation**
 - Please follow the **readme.txt** (Lab3 need to run in **UNIX-like** operating system)
- **Testcase**
 - Lab3Answer/testcase_for_compile.txt

Instruction

Instruction	Example	Meaning	Opcode	Funct3	Funct7
Addition	add r1, r2, r3	$r1 = r2 + r3$	0110011	000	0000000
Subtraction	sub r1, r2, r3	$r1 = r2 - r3$	0110011	000	0100000
Bitwise and	and r1, r2, r3	$r1 = r2 \& r3$	0110011	111	0000000
Bitwise or	or r1, r2, r3	$r1 = r2 r3$	0110011	110	0000000
Exclusive OR	xor r1, r2, r3	$r1 = r2 \oplus r3$	0110011	100	0000000
Set on less than	<u>slt</u> r1, r2, r3	if($r2 < r3$) $r1 = 1$ else $r1 = 0$	0110011	010	0000000
Shift left logical	sll r1, r2, r3	$r1 = r2 \ll r3$	0110011	001	0000000
Shift right arithmetic	sra r1, r2, r3	$r1 = r2 \ggg r3$	0110011	101	0100000

Program Counter

 
- You don't need to implement this part
- Register use to store program counter value



```
module ProgramCounter(  
    input                clk_i,  
    input                rst_i,  
    input [32-1:0] pc_i,  
    output reg [32-1:0] pc_o  
);  
  
always @(posedge clk_i) begin  
    if(~rst_i)  
        pc_o <= 0;  
    else  
        pc_o <= pc_i;  
    end  
endmodule
```

Instruction memory

 - **You don't need to implement this part**
- Fetch instruction by address
- The script we provide will automatically replace the test case



```
`timescale 1ns/1ps

module Instr_Memory(
    input    [32-1:0]    addr_i,
    output wire [32-1:0]    instr_o
);

integer      i;
reg [32-1:0] instruction_file [0:31];

initial begin
    for ( i=0; i<32; i=i+1 )
        instruction_file[i] = 32'b0;
    $readmemb("test_data/C0_test_data10.txt", instruction_file);
end


assign instr_o = instruction_file[addr_i/4];

endmodule
```

Test case


Register file

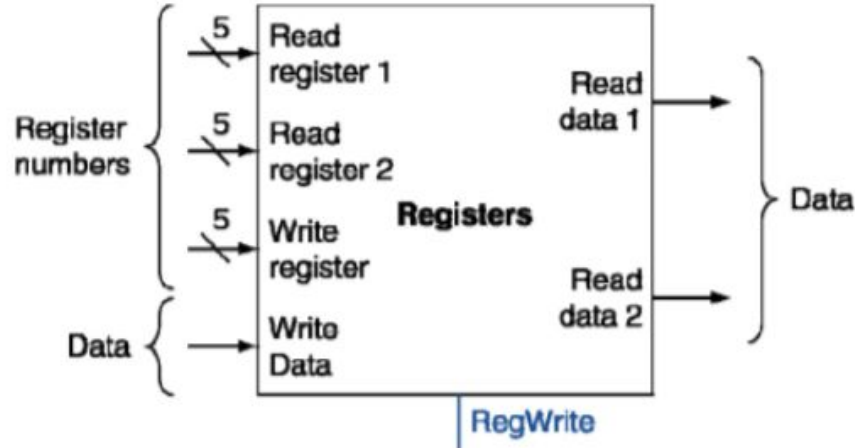- **You don't need to implement this part**
- Consists of a set of registers that can be read and written by supplying a register number to be accessed




PC + 4 Adder

- Increment by 4 for next instruction

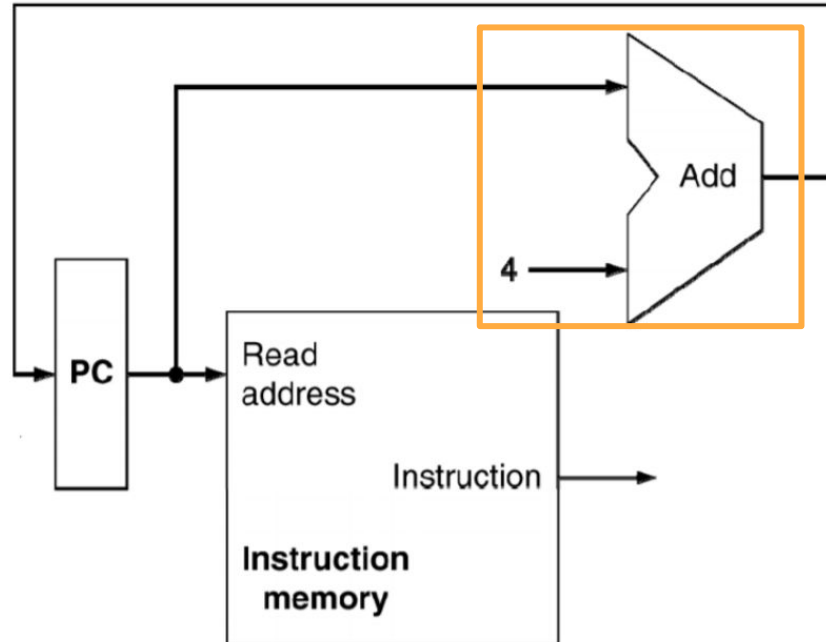


ALU

 - Extend ALU operations (LAB 2) to support more instructions
 - You can use any method to extend ALU operations (e.g. sra, sll, xor)
- ALU performs the corresponding operation depend on ALU control



ALU Control


- You can define **sra**, **sll**, **xor** ALU Control by yourself
- Other R-type instructions ALU Control please follow the table below



opcode	ALUOp	Operation	I ₃₀ +fun3	ALU function	ALU control
ld	00	load register	XXXX	add	0010
sd	00	store register	XXXX	add	0010
beq	01	branch on equal	XXXX	subtract	0110
R-type	10	add	0000	add	0010
		subtract	1000	subtract	0110
		AND	0111	AND	0000
		OR	0110	OR	0001

Decoder

 - Generate the corresponding control signal according to the instruction
- e.g. R-type instructions
 - Branch = ?
 - ALUOp = ?
 - ALUSrc = ?
 - RegWrite = ?



Simple Single CPU

- Combine all the above parts to build a CPU
- You need to complete Simple_Single_CPU.v all the parts input and output

```
ProgramCounter PC(  
    .clk_i(),  
    .rst_i(),  
    .pc_i(),  
    .pc_o()  
);  
  
Instr_Memory IM(  
    .addr_i(),  
    .instr_o()  
);  
  
Reg_File RF(  
    .clk_i(),  
    .rst_i(),  
    .RSaddr_i(),  
    .RTaddr_i(),  
    .RDaddr_i(),  
    .RDdata_i(),  
    .RegWrite_i(),  
    .RSdata_o(),  
    .RTdata_o()  
);
```

Testcase

- Lab3Answer/testcase_for_compile.txt
- In all case, initially
 - **x1 = 1**
 - **x2 = 2**
 - **other = 0**

Case 1 :

```
xor x1,x1,x1
add x2,x2,x1
or x3,x2,x1
sll x4,x3,x2
sub x5,x3,x4
```

result:

x1 = 0 , x2 = 2,x3 = 2 ,x4 = 8 ,x5 = -6

Case 2 :

```
sra x6,x2,x1
sub x4,x4,x2
sub x4,x4,x2
sra x5,x4,x2
```

result:

x1 = 1, x2 = 2,x4 = -4 ,x5 = -1 ,x6 = 1

Testbench

- This script cannot run in Windows
- Put your .v file in Lab3Code
- `$ chmod +x ./lab3TestScript.sh && ./lab3TestScript.sh`

```
***** CASE 1 *****
Testcase 1 PASS
***** CASE 2 *****
Testcase 2 PASS
***** CASE 3 *****
Testcase 3 PASS
***** CASE 4 *****
Testcase 4 PASS
***** CASE 5 *****
Testcase 5 PASS
***** CASE 6 *****
Testcase 6 PASS
***** CASE 7 *****
Testcase 7 PASS
***** CASE 8 *****
Testcase 8 PASS
***** CASE 9 *****
Testcase 9 PASS
***** CASE 10 *****
Testcase 10 PASS
=====
Total Score:100
```

```
***** CASE 1 *****
Case 1 Answer :
r0 = 0, r1 = 0, r2 = 2, r3 = 2,
r4 = 8, r5 = -6, r6 = 0, r7 = 0,
r8 = 0, r9 = 0, r10 = 0, r11 = 0
-----
Your :
r0 = 0, r1 = 2, r2 = 4, r3 = 6,
r4 = 96, r5 = -90, r6 = 0, r7 = 0,
r8 = 0, r9 = 0, r10 = 0, r11 = 0
Testcase 1 WRONG
***** CASE 2 *****
Testcase 2 PASS
***** CASE 3 *****
Testcase 3 PASS
***** CASE 4 *****
Testcase 4 PASS
***** CASE 5 *****
Testcase 5 PASS
***** CASE 6 *****
Testcase 6 PASS
***** CASE 7 *****
```