

Lab2: 32-bit ALU

TA-黃威淳

s094398.cs10@nycu.edu.tw

Tool

- **Icarus verilog**

- Mac OSX
 - `brew install icarus-verilog`
- Windows
 - https://bleyer.org/icarus/iverilog-v11-20210204-x64_setup.exe
- Ubuntu
 - `sudo apt install verilog`

- **GTKWave (unnecessary)**




- Easy to debug

- **Other HDL simulator (unnecessary)**

- Easy for debug

Attached file

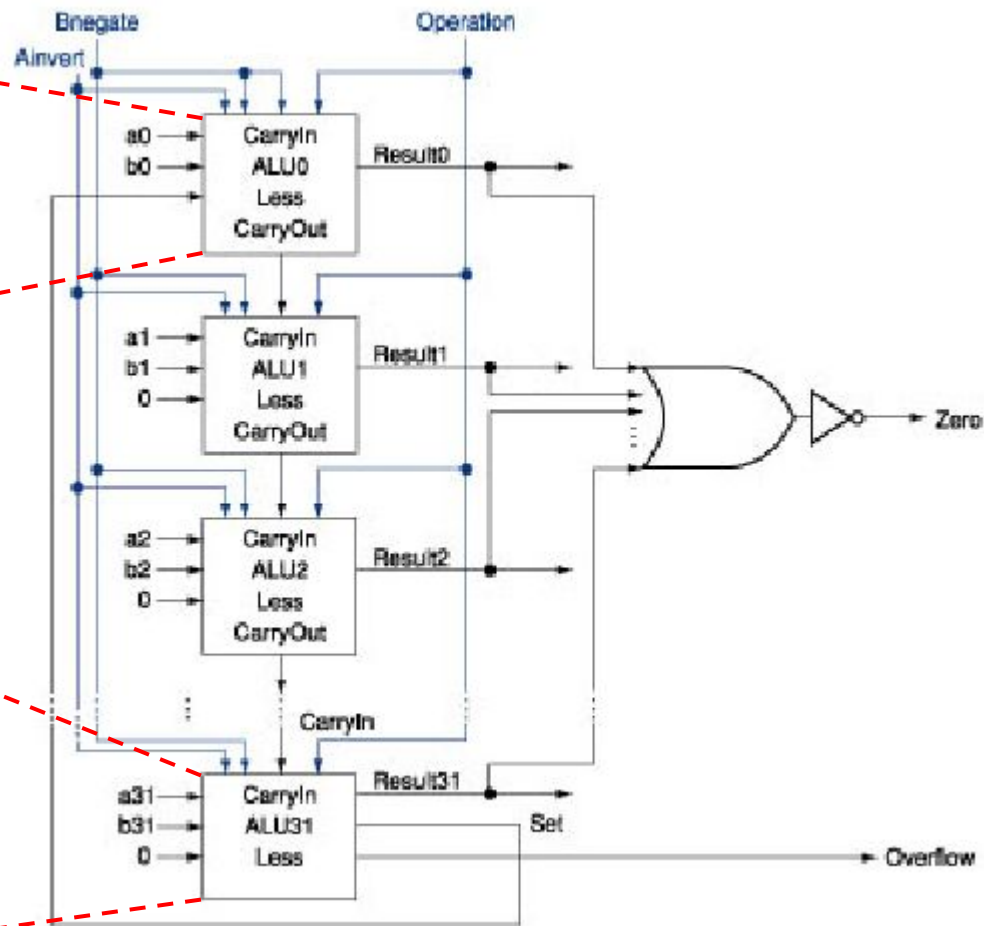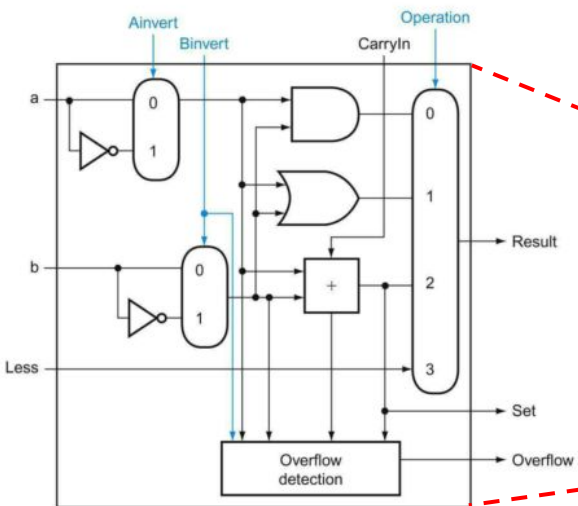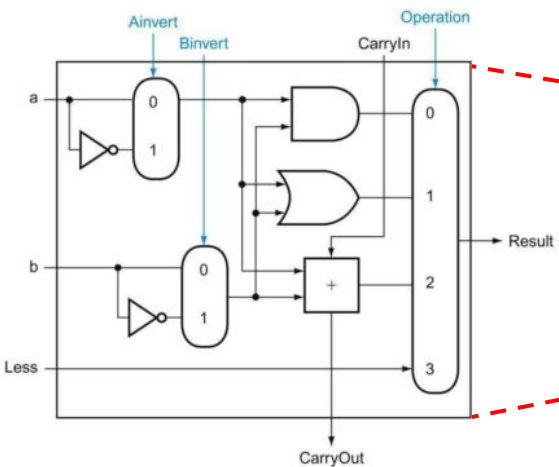- **TODO**
 - alu.v (32-bit ALU)
 - alu_1bit.v
 - MUX2to1.v
 - MUX4to1.v
 - **Validate the correction of your implementation (32 bit ALU)**
 - testbench.v
 - **Testcase**
 - *.txt
 - **Simple testbench (1 bit ALU)**
 - alu_1bit_tb.v
- Please do not modify these files




MUX 2to1 & 4to1

```
module MUX2to1(  
    input    src1,  
    input    src2,  
    input    select,  
    output reg result  
);  
/* Write your code HERE */  
endmodule
```

```
module MUX4to1(  
    input    src1,  
    input    src2,  
    input    src3,  
    input    src4,  
    input    [2-1:0] select,  
    output reg result  
);  
/* Write your code HERE */  
endmodule
```

1 Bit ALU

 

```
timescale 1ns/1ps

module alu_1bit(
    input src1,           //1 bit source 1 (input)
    input src2,           //1 bit source 2 (input)
    input less,           //1 bit less (input)
    input Ainvert,        //1 bit A_invert (input)
    input Binvert,        //1 bit B_invert (input)
    input cin,            //1 bit carry in (input)
    input [2-1:0] operation, //2 bit operation (input)
    output reg result,    //1 bit result (output)
    output reg cout       //1 bit carry out (output)
);

/* Write your code HERE */

endmodule
```

The diagram illustrates a multi-ALU datapath architecture. It consists of 32 ALU units, labeled ALU0 through ALU31. Each ALU unit has four inputs: a CarryIn, and three data inputs (a0, b0, and an Operation). The outputs of each ALU are Result0 through Result31. A Zero flag is generated by an OR gate combining the Zero flags of all ALUs. An Overflow flag is generated by an OR gate combining the Overflow flags of all ALUs. A Set flag is generated by an AND gate combining the Set flags of all ALUs. The CarryIn of ALU0 is the global CarryIn, and the CarryOut of ALU31 is the global CarryOut.

```
timescale 1ns/1ps

module alu(
    input          rst_n,          // negative reset                (input)
    input          [32-1:0] src1,  // 32 bits source 1          (input)
    input          [32-1:0] src2,  // 32 bits source 2          (input)
    input          [ 4-1:0] ALU_control, // 4 bits ALU control input (input)
    output reg     [32-1:0] result, // 32 bits result            (output)
    output reg     zero,          // 1 bit when the output is 0, zero (output)
    output reg     cout,          // 1 bit carry out            (output)
    output reg     overflow       // 1 bit overflow              (output)
);

/* Write your code HERE */

endmodule
```

Testbench - 1 bit

Your code

- \$ iverilog -o 1bit alu_1bit_tb.v alu_1bit.v MUX*

output file (default: a.out)

- \$./1bit
- We provide simple 1-bit ALU testbench, feel free to use it !
- Just for testing your 1-bit ALU correctness

```
sum x
carry x
=====
sum x
carry x
=====
sum x
carry x
=====
```

alu_1bit_tb.v

```
initial // initial block executes only once
begin
```

```
// values for a and b
```

```
a = 1;
b = 1;
less = 0;
Ainvert = 0;
Binvert = 0;
cin = 0;
operation = 2'b00;
```

You can modify these value

```
#1
$display("sum %d", sum);
$display("carry %d", carry);
$display("=====");
#period; // wait for period
```

```
a = 1;
b = 1;
less = 0;
Ainvert = 0;
Binvert = 0;
cin = 0;
operation = 2'b01;
```

```
#1
$display("sum %d", sum);
$display("carry %d", carry);
$display("=====");
#period;
```

```
a = 1;
b = 1;
less = 0;
Ainvert = 0;
Binvert = 0;
cin = 0;
operation = 2'b11;
```

```
#1
$display("sum %d", sum);
$display("carry %d", carry);
$display("=====");
#period;
```

```
end
```


Testbench

Your code



- `$ iverilog -o lab2 alu.v alu_1bit.v testbench.v MUX*`



output file (default: a.out)

- `$./lab2`
- Do not modify testbench.v

```
*****
*                PATTERN RESULT TABLE                *
*****
* PATTERN *          Result          * ZCV *
*****
* No. 1 error! *
* Correct result: eeeeeeee      Correct ZCV: 000 *
* Your result: xxxxxxxx        Your ZCV: xxx *
*****
* No. 2 error! *
* Correct result: 00000000      Correct ZCV: 100 *
* Your result: xxxxxxxx        Your ZCV: xxx *
*****
* No. 3 error! *
* Correct result: 9bf5fea6      Correct ZCV: 000 *
* Your result: xxxxxxxx        Your ZCV: xxx *
*****
* No. 4 error! *
* Correct result: 00000000      Correct ZCV: 110 *
* Your result: xxxxxxxx        Your ZCV: xxx *
*****
* Congratulation! All data are correct! *
*****
Correct Count: 30
```

```
*****
*                PATTERN RESULT TABLE                *
*****
* PATTERN *          Result          * ZCV *
*****
* No. 1 error! *
* Correct result: eeeeeeee      Correct ZCV: 000 *
* Your result: xxxxxxxx        Your ZCV: xxx *
*****
* No. 2 error! *
* Correct result: 00000000      Correct ZCV: 100 *
* Your result: xxxxxxxx        Your ZCV: xxx *
*****
* No. 3 error! *
* Correct result: 9bf5fea6      Correct ZCV: 000 *
* Your result: xxxxxxxx        Your ZCV: xxx *
*****
* No. 4 error! *
* Correct result: 00000000      Correct ZCV: 110 *
* Your result: xxxxxxxx        Your ZCV: xxx *
*****
```

Testcase

- testcase.txt
 - 30 cases

number	OP	function	src1	src2	result	zcv
1	d	NAND	11111111	11111111	eeeeeeee	000
2	0	AND	ffff0000	0000ffff	00000000	100
3	1	OR	9284fc02	8b71d6a6	9bf5fea6	000
4	2	ADD	ffffffff	00000001	00000000	110
5	2	ADD	7fffffffff	7fffffffff	fffffffe	001
6	6	SUB	c4fab894	54b51e1e	70459a76	011
7	6	SUB	76543210	01234567	7530eca9	010
8	7	SLT	00000000	0fffffffff	00000001	000
9	C	NOR	00000000	00000000	ffffffff	000
10	2	ADD	00000000	00000000	00000000	100
11	2	ADD	00000000	ffffffff	ffffffff	000
12	2	ADD	00000001	ffffffff	00000000	110
13	6	SUB	00000000	00000000	00000000	110
14	6	SUB	00000000	ffffffff	00000001	000
15	6	SUB	00000001	00000001	00000000	110
16	6	SUB	00000100	00000001	000000ff	010
17	7	SLT	00000000	00000000	00000000	100
18	7	SLT	00000000	00000001	00000001	000
19	7	SLT	00000000	ffffffff	00000000	100
20	7	SLT	00000001	00000000	00000000	100
21	7	SLT	ffffffff	00000000	00000001	000
22	0	AND	ffffffff	ffffffff	ffffffff	000
23	0	AND	ffffffff	12345678	12345678	000
24	0	AND	12345678	87654321	02244220	000
25	0	AND	00000000	ffffffff	00000000	100
26	1	OR	ffffffff	ffffffff	ffffffff	000
27	1	OR	12345678	87654321	97755779	000
28	1	OR	00000000	ffffffff	ffffffff	000
29	1	OR	00000000	00000000	00000000	100
30	d	NAND	00000000	ffffffff	ffffffff	000

How to debug

- 1-bit ALU
 - `$ iverilog -o 1bit alu_1bit_tb.v alu_1bit.v MUX*`
 - `$./1bit`
 - You will get **alu_1bit.vcd** and open it with GTKWave
- 32-bit ALU
 - `$ iverilog -o lab2 alu.v alu_1bit.v testbench.v MUX*`
 - `$./lab2`
 - You will get **alu.vcd** and open it with GTKWave

Hint

Verilog `generate & for` may help you to finish this lab